

EE517: ANALOG IC DESIGN LAB

Analog IC Design Project

Design and analysis of a 2-stage op-amp.



Submitted by,

AILA TEJ RITHVIK - 244102401

CHINNAPOGULA DINESH - 244102405

THAMADA ANKITA - 244102414

EEE - VLSI & NANOELECTRONICS

Contents

1	Project	3
1.1	General Specification:	3
1.2	Targeted Outcomes:	3
2	Theory	4
2.1	Introduction	4
2.2	First Stage: Differential Amplifier	4
2.3	Second Stage: Gain Stage (CS Amplifier)	4
3	Literature Review	5
3.1	Drawbacks of Traditional Design Methodology	5
3.2	gm/Id Methodology	5
3.3	Using gm/Id Charts for Circuit Design	6
4	MOSFET Characterization	7
4.1	Simulation Setup	7
4.2	Procedure	8
4.3	NMOS Characterization Plots	8
4.3.1	Plots w.r.t V_{GS}	8
4.3.2	g_m/I_D Plots	10
4.4	PMOS Characterization Plots	12
4.4.1	Plots w.r.t V_{GS}	12
4.4.2	g_m/I_D Plots	14
5	Hand Calculations	16
6	Two Stage Op-amp Design Procedure	18
6.1	Problem Statement	18
6.2	Schematic	19
6.3	Design Methodology	19
6.4	Device Size Calculation	20
6.5	Miller Compensation	20
6.6	Design Summary	22
7	Simulation Results	23
7.1	DC Analysis	23
7.1.1	ICMR and OCMR	23
7.1.2	Output Swing	23
7.2	Summary of DC Parameters	24
7.3	AC Analysis	25
7.3.1	Gain and 3dB Bandwidth	25
7.3.2	Unity Gain Frequency	26
7.3.3	Phase Margin	27
7.3.4	Common Mode Gain	28
7.3.5	PSRR	29
7.4	Transient Analysis	30
7.4.1	Slew rate	30

1 Project

Design a 2-stage Op-amp in 180 nm technology targeting different target specifications by gm/Id methodology. The following are the general requirements for an Amplifier.

1. High Gain
2. High Gain Band Width (GBW)
3. Low area
4. Low Power

1.1 General Specification:

- Supply voltage (V_{DD}) = 1.8 V
- Reference current source (I_{ref}) = 20 μ A
- Slew rate = 1 V/ μ s
- Phase margin $\geq 60^\circ$
- Load capacitance (C_L) = 1 pF
- Input Common Mode Range (ICMR) = 0.6-1.4 V

1.2 Targeted Outcomes:

- High Gain Bandwidth (GBW)
- Gain ≥ 40 dB
- GBW ≥ 70 MHz
- Power Dissipation (P_{diss}) ≤ 1 mW
- Maximum Length (L_{max}) ≤ 2 μ m

2 Theory

2.1 Introduction

A two-stage operational amplifier consists of two cascaded amplification stages to achieve high gain while maintaining a reasonable output voltage swing. It is commonly used in analog circuit design due to its flexibility and performance.

2.2 First Stage: Differential Amplifier

The first stage is a differential amplifier with an active load, responsible for the following Operation:

- Amplifying the differential input signal.
- Attenuating Common Mode signals.
- Providing high gain.
- Converting the differential signal to a single-ended signal.

This stage includes input transistors (M1, M2), active load transistors (M3, M4), and a current source (M5, M8) for biasing.

2.3 Second Stage: Gain Stage (CS Amplifier)

The second stage is a common-source amplifier formed by M6, which further amplifies the signal and drives the output load.

Key Benefits

- Increases the overall gain of the op-amp.
- Provides a better voltage swing at the output compared to a single-stage amplifier.

 


Figure 1: Two Stage Opamp

3 Literature Review

3.1 Drawbacks of Traditional Design Methodology

Traditional approaches to analog IC design often rely on simplified square-law equations for MOSFET behavior, assuming ideal conditions that neglect various second-order effects. These shortcomings include:

1. Ignoring short-channel effects such as velocity saturation and drain-induced barrier lowering.
2. Neglecting the dependence of threshold voltage (V_{TH}) on device dimensions such as Width and Length of the Channel and bias conditions.
3. Threshold Voltage also depends heavily on Source Node Voltage, assuming all the Body Terminals are connected to either Vdd (for PMOS) and gnd (for NMOS).
4. Oversimplification of channel-length modulation, leading to inaccuracies in gain calculations.

Such assumptions result in significant discrepancies between theoretical predictions and actual performance, particularly for modern sub-micron processes. To overcome these limitations, the gm/Id methodology offers a more accurate and comprehensive approach to transistor characterization and design.

3.2 gm/Id Methodology

The gm/Id methodology provides a systematic framework for analog circuit design by directly leveraging the transconductance efficiency (gm/I_d) as a key design parameter. This approach involves the following steps:

1. Characterize MOSFETs by simulating various operating points to obtain the following plots:
 - Transconductance (gm) versus gate-source voltage (V_{GS}).
 - Drain current (I_d) versus gate-source voltage (V_{GS}).
 - Transconductance efficiency (gm/I_d) versus gate-source voltage (V_{GS}).
2. Extract derived parameters such as:
 - Intrinsic gain: $\frac{gm}{g_{ds}}$, representing the maximum achievable gain.
 - Transit frequency: $\frac{gm}{2\pi C_{gs}}$, indicating the bandwidth potential.
3. Use these plots to design devices for optimal performance metrics tailored to the application requirements.

The gm/Id charts serve as lookup tables, enabling precise calculations and bridging the gap between simulation results and analytical design.

g_m/I_D Design Flow

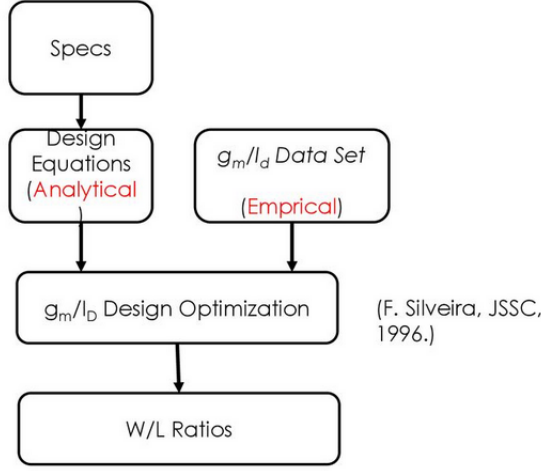


Figure 2: Flow Chart of g_m/I_D Methodology

3.3 Using g_m/I_D Charts for Circuit Design

The g_m/I_D methodology simplifies analog circuit design by leveraging the efficiency of transconductance-to-current ratio (g_m/I_d). This parameter remains largely independent of the transistor's aspect ratio when the gate overdrive voltage ($V_{GS} - V_{TH}$) is greater than zero. Key considerations for implementing this approach include:

1. Selection of g_m/I_D Values:

- A smaller g_m/I_D is suitable for devices that do not contribute directly to gain, such as active loads, or when compact area and high speed are desired.
- A larger g_m/I_D is preferable for gain-contributing devices, such as the input stage of an amplifier, or when low flicker noise, better mismatch, and large voltage swings are required.

2. Device Parameters:

- Drain current (I_d): Chosen based on the power budget.
- Channel length (L): Set to ensure that intrinsic gain (g_m/g_{ds}) meets the required specifications. Excessive values of g_m/g_{ds} may lead to reduced bandwidth due to lower f_T , necessitating careful trade-off analysis.
- Width (W): Determined from the I_d/W versus g_m/I_d chart after selecting I_d .
- DC Operating Voltage: Extracted from the g_m/I_d versus V_{OV} chart to ensure consistent operation at the specified g_m/I_d value.

This systematic design approach bridges the gap between theoretical insights and practical implementation, providing a robust framework for achieving optimal circuit performance.

4 MOSFET Characterization

4.1 Simulation Setup

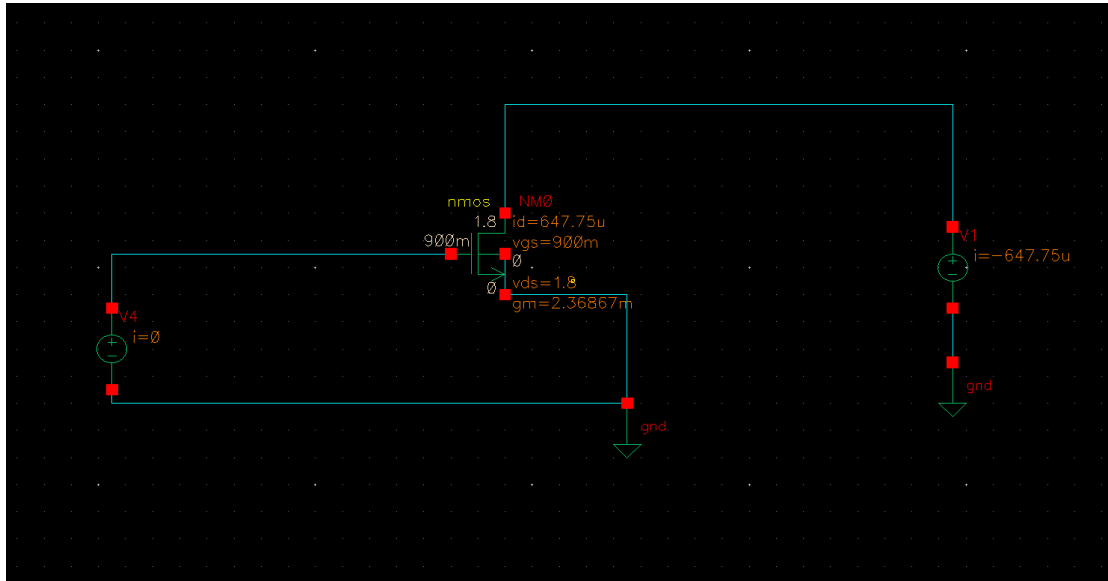


Figure 3: Schematic of NMOS characterization simulation setup

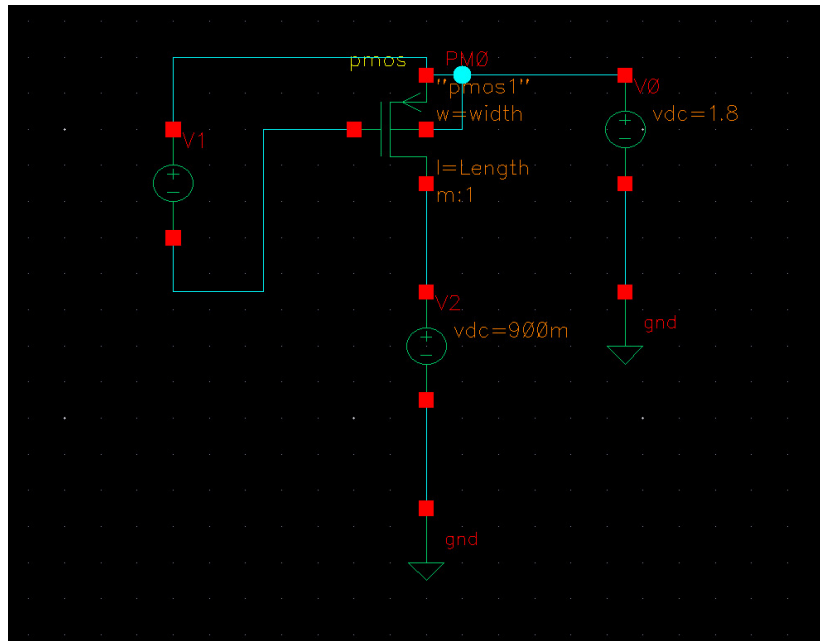


Figure 4: Schematic of PMOS characterization simulation setup

4.2 Procedure

- **Step 1:** Plot I_D , g_m , g_m/I_D , f_T , g_m/g_{ds} , V_{ov} and I_D/W versus V_{GS} .
- **Step 2:** From the above data, the g_m/I_D charts can be generated for the PMOS and NMOS transistors. These include the following plots:
 1. g_m/I_D versus V_{ov}
 2. f_T versus g_m/I_D
 3. g_m/g_{ds} versus g_m/I_D
 4. I_D/W versus g_m/I_D

4.3 NMOS Characterization Plots

4.3.1 Plots w.r.t V_{GS}

 


Figure 5: Drain current (I_D) vs V_{GS}

 


Figure 6: Transconductance (g_m) vs V_{GS}

 


Figure 7: Transconductance efficiency (g_m/I_D) vs V_{GS}

 


Figure 8: Transition frequency (f_T) vs V_{GS}

4.3.2 g_m/I_D Plots

 


Figure 9: g_m/I_D vs V_{OV}

 


Figure 10: f_T vs g_m/I_D

 


Figure 11: $f_T \cdot (g_m/I_D)$ vs g_m/I_D

 


Figure 12: g_m/g_{ds} vs g_m/I_D

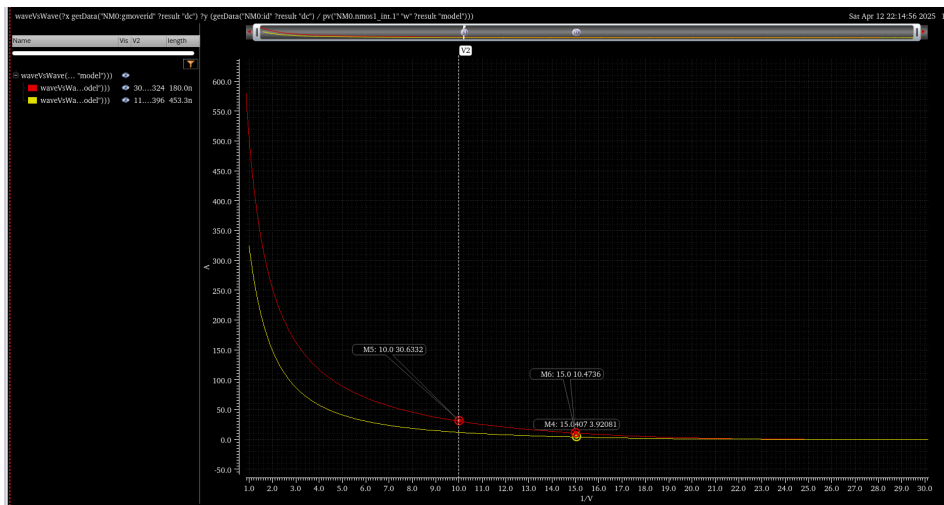


Figure 13: I_D/W vs g_m/I_D

4.4 PMOS Characterization Plots

4.4.1 Plots w.r.t V_{GS}

 


Figure 14: Drain current (I_D) vs V_{GS}

 


Figure 15: Transconductance (g_m) vs V_{GS}

 


Figure 16: Transconductance efficiency (g_m/I_D) vs V_{GS}

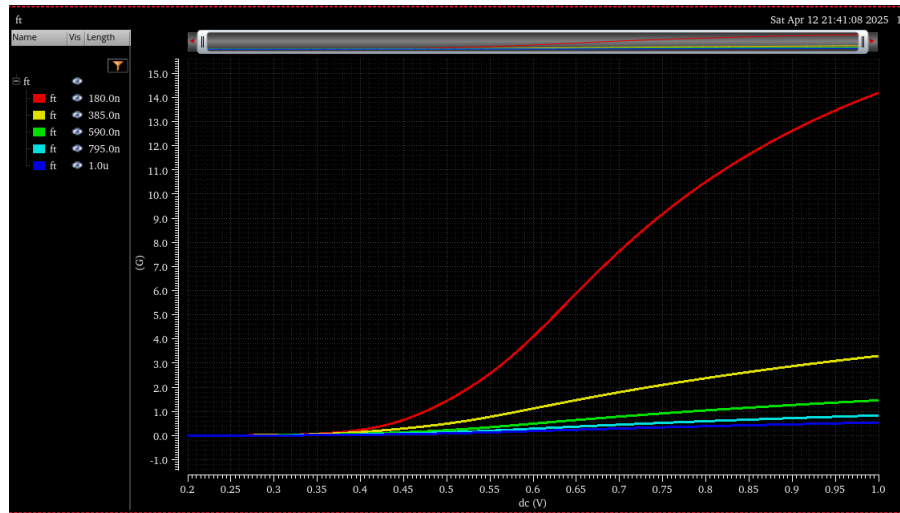


Figure 17: Transition frequency (f_T) vs V_{GS}

4.4.2 g_m/I_D Plots

 


Figure 18: g_m/I_D vs V_{OV}

 


Figure 19: f_T vs g_m/I_D

 


Figure 20: $f_T \cdot (g_m/I_D)$ vs g_m/I_D

 


Figure 21: g_m/g_{ds} vs g_m/I_D

 


Figure 22: I_D/W vs g_m/I_D

5 Hand Calculations

Two-Stage Op-Amp Design Calculations

Step 1: Compensation Capacitor (C_c) Selection

Given:

$$C_L = 1 \text{ pF}$$

Theoretical calculation for a phase margin of 60 degrees in a two-stage op-amp:

$$C_c \geq 0.22 \cdot C_L \Rightarrow C_c \geq 0.22 \cdot 1 \text{ pF} = 220 \text{ fF}$$

We select slightly higher value of C_c considering the effect of parasitic capacitance,

$$C_c = 330 \text{ fF}$$

Step 2: Transconductance Calculations for Required GBW

Given:

$$\text{Target GBW} \geq 70 \text{ MHz, Assume } GBW = 100 \text{ MHz}$$

For a two-stage op-amp:

Input Transconductance g_{m1}

$$\begin{aligned} g_{m1} &= 2\pi \cdot GBW \cdot C_c = 2\pi \cdot 100 \times 10^6 \text{ Hz} \cdot 330 \times 10^{-15} \text{ F} \\ g_{m1} &= 207.345 \text{ } \mu\text{A/V} \end{aligned}$$

Second Stage Transconductance g_{m2}

$$\begin{aligned} g_{m2} &\geq 2.2 \cdot 2\pi \cdot GBW \cdot C_L = 2.2 \cdot 2\pi \cdot 100 \times 10^6 \text{ Hz} \cdot 1 \times 10^{-12} \text{ F} \\ g_{m2} &= 1381.6 \text{ } \mu\text{A/V} \end{aligned}$$

Step 3: Bias Currents Using g_m/I_D

Assumed:

- $g_m/I_D = 15$ for M_1 , M_2 , and M_6
- $g_m/I_D = 10$ for all other transistors

Currents for M_1 , M_2

$$\begin{aligned} I_{D1} &= \frac{g_{m1}}{g_m/I_D} = \frac{207.345 \text{ } \mu\text{A/V}}{15} = 13.823 \text{ } \mu\text{A} \\ I_{D2} &= I_{D1} = 13.823 \text{ } \mu\text{A} \end{aligned}$$

Current for M_6

$$I_{D6} = \frac{g_{m2}}{g_m/I_D} = \frac{1381.6 \text{ } \mu\text{A/V}}{15} = 92.1066 \text{ } \mu\text{A}$$

Step 4: Transistor Sizing Using I_D/W Graph

From the graph of I_D/W vs g_m/I_D :

- For $g_m/I_D = 15$, $I_D/W = 10.4736$ for M_1, M_2 (NMOS)
- For $g_m/I_D = 15$, $I_D/W = 2.56264$ for M_6 (PMOS)
- For $g_m/I_D = 10$, $I_D/W = 7.6443$ for M_3, M_4 (PMOS)
- For $g_m/I_D = 10$, $I_D/W = 30.633$ for M_5 (NMOS)

Widths of M_1, M_2

$$W_1 = W_2 = \frac{I_{D1}}{I_D/W} = \frac{13.823 \mu\text{A}}{10.4736} = 1.32 \mu\text{m}$$

Width of M_6

$$W_6 = \frac{I_{D6}}{I_D/W} = \frac{92.1066 \mu\text{A}}{2.56264} = 35.94 \mu\text{m}$$

Widths of M_3, M_4

$$W_3 = W_4 = \frac{I_{D3}}{I_D/W} = \frac{13.823 \mu\text{A}}{7.6443} = 1.808 \mu\text{m}$$

Width of M_5

$$I_{D5} = I_{D1} + I_{D2} = 27.646 \mu\text{A}$$
$$W_5 = \frac{I_{D5}}{I_D/W} = \frac{27.646 \mu\text{A}}{30.633} = 0.9025 \mu\text{m}$$

Width of M_7

$$W_7 = \frac{I_{D7}}{I_D/W} = \frac{92.1066 \mu\text{A}}{7.6433} = 12.048 \mu\text{m}$$

Step 5: Channel Length Selection

As per the g_m/g_{ds} vs g_m/I_D graph, we choose the channel length for all transistors as:

$$L = 180 \text{ nm}$$

6 Two Stage Op-amp Design Procedure

6.1 Problem Statement

 


Figure 23: Circuit Diagram of Two Stage Op-amp

Design a basic two-stage op-amp based on the following specifications:

- Open loop voltage gain $\geq 40dB$
- Unity gain frequency $\geq 70MHz$
- Phase margin $\geq 60^\circ$
- ICMR : 0.6V - 1.4V
- Power dissipation $\leq 1mW$

Consider $V_{DD} = 1.8V$ and load capacitance $C_L = 1pF$.

6.2 Schematic

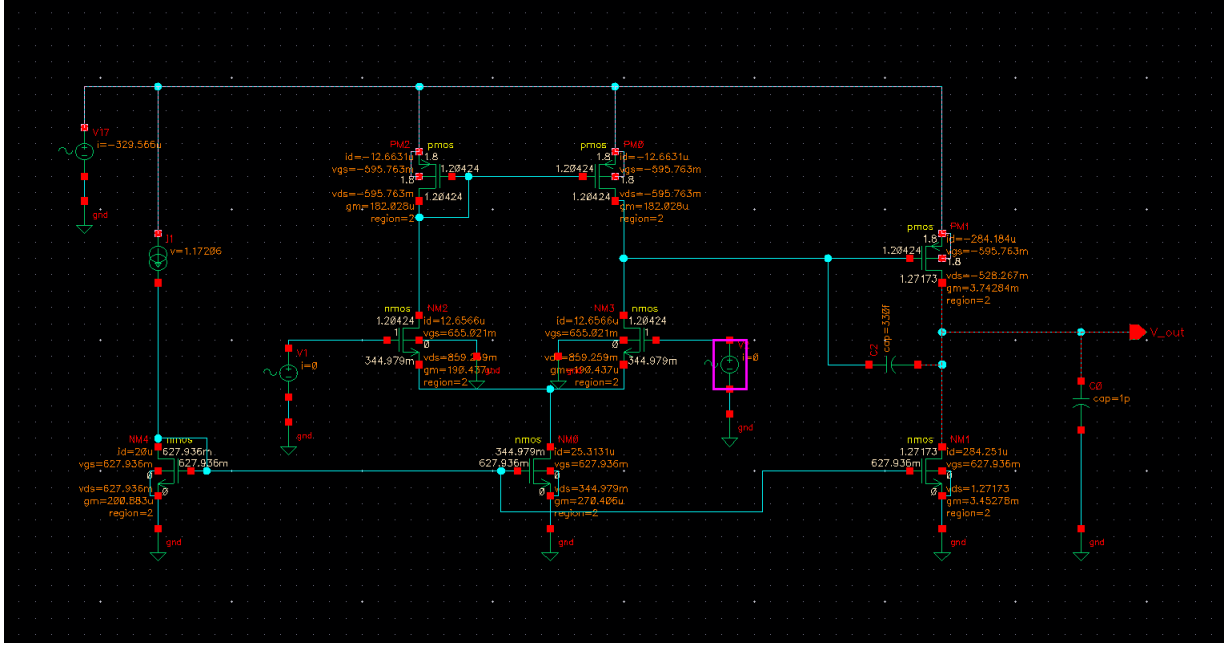


Figure 24: Schematic in Cadence of Two Stage Op-amp

6.3 Design Methodology

The design process for the two-stage operational amplifier involves the following key steps:

1. Determine the g_m/I_d values for each transistor. These are generally chosen between 10 and 20, based on their specific roles in the circuit.
2. For transistors contributing to the gain (M_1, M_2, M_6), higher g_m/I_d values are preferred, while current source load transistors benefit from lower values.
3. Begin the design by assigning typical g_m/I_d values: 15 for gain-contributing transistors and 10 for others.
4. Select transistor lengths based on g_m/g_{ds} versus g_m/I_d curves for various channel lengths. Hand calculations can help determine the minimum length that meets gain requirements.
5. Use the power budget to calculate current through each transistor, deriving transistor widths from the I_d/W versus g_m/I_d chart.
6. Verify bandwidth requirements by consulting the f_T versus g_m/I_d curve for the chosen L and g_m/I_d .
7. Once transistor dimensions are finalized, obtain bias voltages using g_m/I_d versus V_{ov} charts.

6.4 Device Size Calculation

1. The total power consumption is set to 1mW, corresponding to a bias current limit of $550\mu\text{A}$. A current mirror biasing strategy is applied, allocating $20\mu\text{A}$ to the bias transistor. The tail current for the differential stage and the current for the common-source stage are set to $27.5\mu\text{A}$ and $92.10\mu\text{A}$ respectively.
2. Aiming for an open-loop gain of 100, assuming differential stage gain to be 10 and common source stage gain to be 10. the intrinsic gain (g_m/g_{ds}) is at 20. Transistor length L is initially chosen 180nm as minimum channel length yielded the required gain.
3. For transistors M_1 and M_2 , the I_d/W ratio derived from g_m/I_d charts (at $g_m/I_d = 15$) is 10.4736, leading to $W_{M_1} = W_{M_2} = 1.31823\mu\text{m}$.
4. For M_3 and M_4 , the I_d/W ratio at $g_m/I_d = 10$ is 7.64435, giving $W_{M_3} = W_{M_4} = 1.80\mu\text{m}$.
5. For M_6 with I_d/W at $g_m/I_d = 15$ being 2.56264, the width is $W_{M_6} = 35.94\mu\text{m}$.
6. For M_7 with I_d/W at $g_m/I_d = 10$ being 7.64435, the width is $W_{M_7} = 12.048\mu\text{m}$.
7. For M_5 with I_d/W at $g_m/I_d = 10$ being 30.63324, the width is $W_{M_5} = 900\text{nm}$.

6.5 Miller Compensation

Assuming p_1, p_2 denote the dominant poles, z the zero, GBP the gain-bandwidth product, and PM the phase margin of the op-amp, we calculate:

$$PM = 180^\circ - \tan^{-1}\left(\frac{GBP}{p_1}\right) - \tan^{-1}\left(\frac{GBP}{p_2}\right) - \tan^{-1}\left(\frac{GBP}{z}\right) \quad (1)$$

Given $\tan^{-1}\left(\frac{GBP}{p_1}\right) \approx 90^\circ$, we require $p_2 = 2.2GBP$ for a 60° phase margin. Using:

Where,

$$p_1 = \frac{1}{g_{m6}R_1R_2C_c}$$

$$p_2 = \frac{g_{m6}}{2\pi C_L}$$

$$z = \frac{g_{m6}}{2\pi C_c}$$

Assumption:

- As zero is right hand plane zero, it makes the system unstable. It adds -90° to phase margin hence it should be atleast 10 times of GBP. To minimize its effect on phase margin.

Phase Margin Calculation:

$$PM = 180^\circ - \tan^{-1} \left(\frac{GBP}{p_1} \right) - \tan^{-1} \left(\frac{GBP}{p_2} \right) - \tan^{-1} \left(\frac{GBP}{z} \right) \quad (2)$$

Where,

$$\tan^{-1} \left(\frac{GBP}{z} \right) = 5.71^\circ$$

$$PM = 180^\circ - 90^\circ - 5.71^\circ - \tan^{-1} \left(\frac{GBP}{P_2} \right)$$

Thus,

$$PM = 84.29^\circ - \tan^{-1} \left(\frac{GBP}{P_2} \right)$$

For a desired phase margin of 60° :

$$\frac{GBP}{P_2} = \tan(24.29^\circ)$$

$$\frac{GBP}{P_2} = 0.4153$$

$$P_2 \geq 2.2 \times GBP$$

Hence, P_2 should be at least $2.2 \times GBP$ for a phase margin of 60° .

$$P_2 = \frac{g_{m6}}{2\pi C_L}$$

$$GBP = \frac{g_{m1}}{2\pi C_C}$$

$$P_2 = \frac{g_{m6}}{2\pi C_L}$$

$$GBP = \frac{g_{m1}}{2\pi C_L}$$

$$\frac{g_{m6}}{2\pi C_L} \geq 2.2 \left(\frac{g_{m1}}{2\pi C_L} \right)$$

$$g_{m6} \geq 10g_{m1}$$

As mentioned above,

$$g_{m6} \geq 10g_{m1}$$

$$C_c \geq 0.22C_L$$

6.6 Design Summary

Below is the summary of the device dimensions and operating conditions:


Device	L (nm)	W (μm)	g_m/I_d (V^{-1})	I_d (μA)
M_1	180	1.3	15.17	12.657
M_2	180	1.3	15	12.657
M_3	180	4.54	14.376	12.657
M_4	180	4.54	14.376	12.657
M_5	1000	6.02	10.683	25.314
M_6	180	72	14.17	284.178
M_7	180	15	12.1	284.178

Table 1: Device dimensions and operating currents

7 Simulation Results

7.1 DC Analysis


7.1.1 ICMR and OCMR

 


ICMR	851.163mV - 1.702V
OCMR	1.233V - 1.316V

7.1.2 Output Swing

At input common mode voltage of 850mV

 

At input common mode voltage of 1.4V

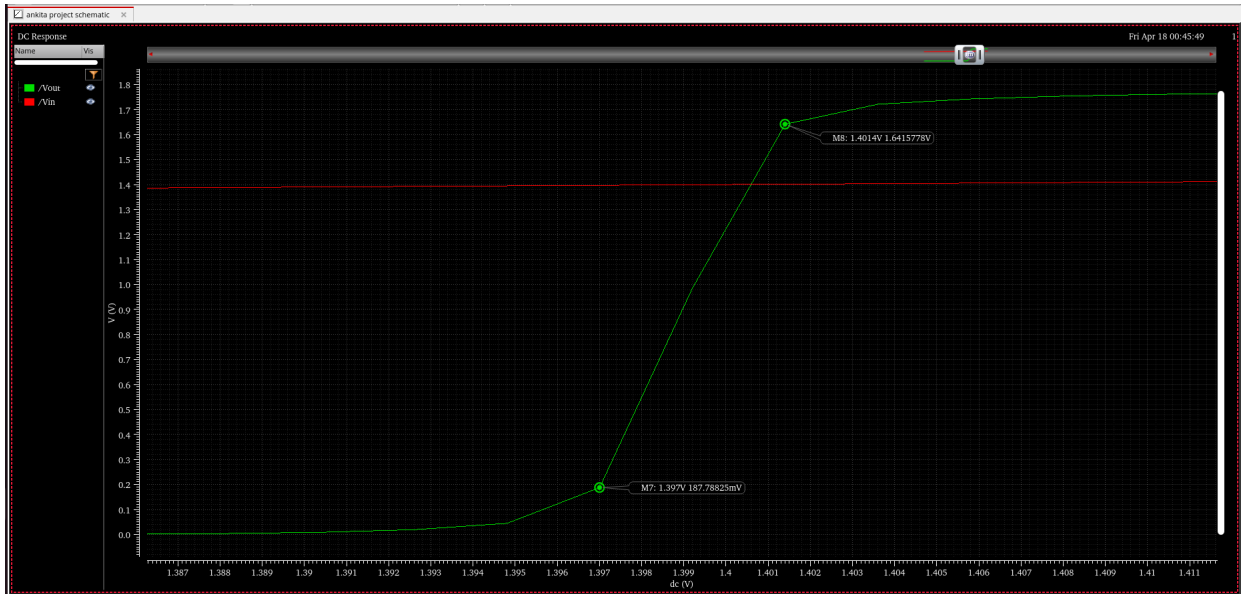

Input Common Mode Voltage	Output Swing
850mV	156.582mV - 1.6343V
1.4V	187.788mV - 1.6415V

7.2 Summary of DC Parameters


The DC performance parameters of the op-amp as obtained from the DC analysis are enlisted below:

1. DC differential-mode gain = 794
2. DC common-mode gain = 0.48
3. Worst case CMRR = 64.25 dB
4. Lower saturation limit = 74.73mV
5. Upper saturation limit = 1.72 V
6. Power dissipation = 581 μ W


7.3 AC Analysis

7.3.1 Gain and 3dB Bandwidth

At input common mode voltage of 850mV

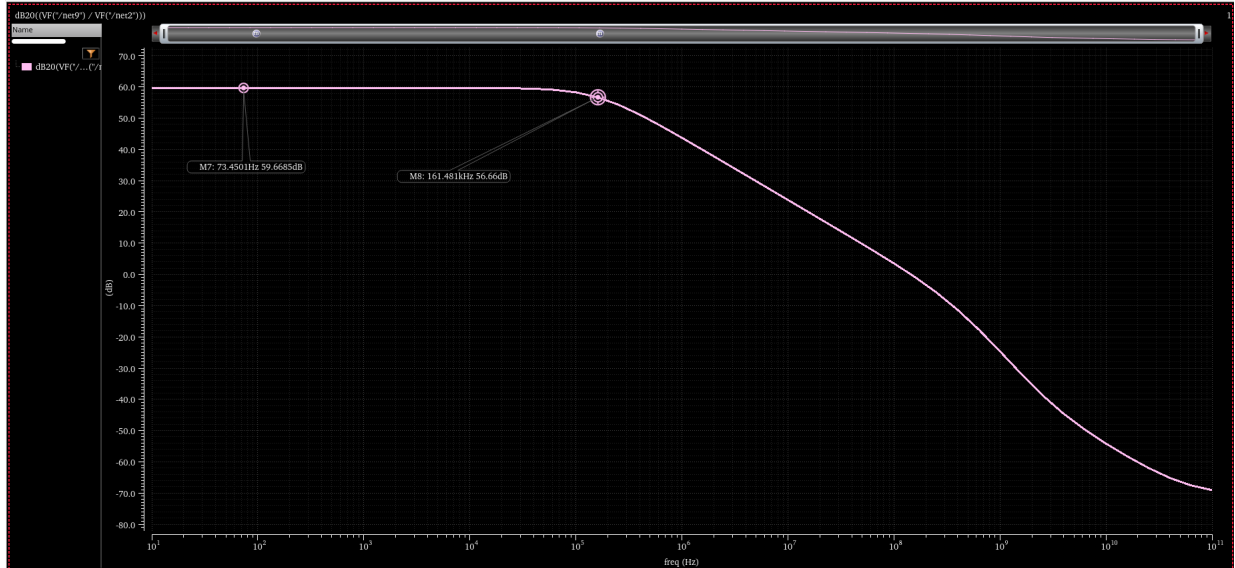


At input common mode voltage of 1.4V

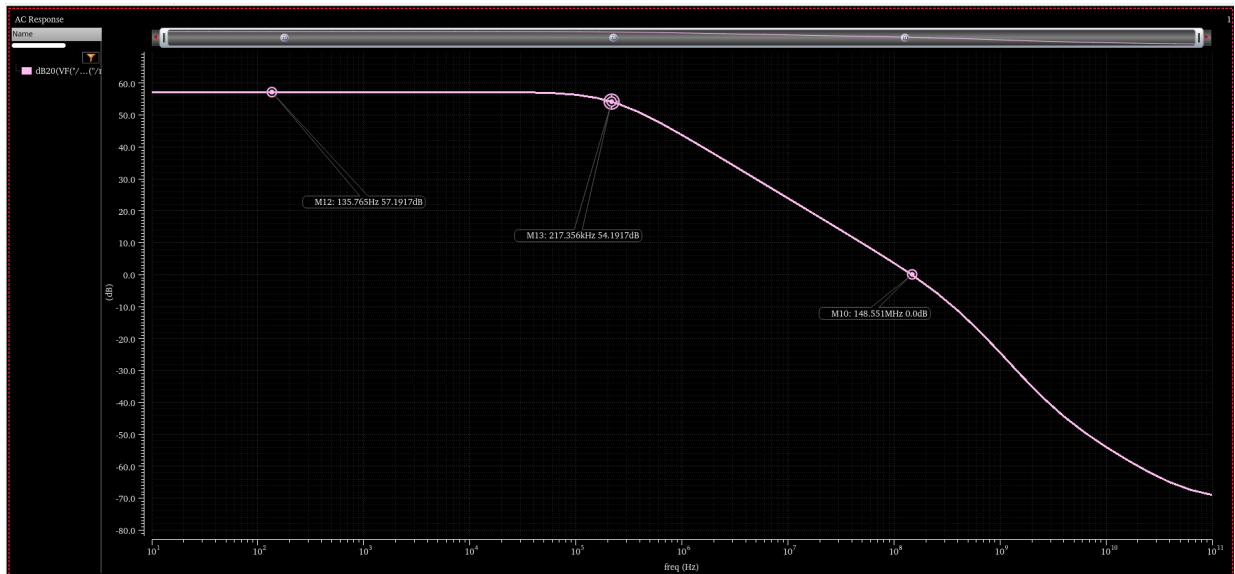


Input Common Mode Voltage	Gain	3dB Bandwidth
850mV	59.6685 dB	161.481 kHz
1.4V	57.1917 dB	217.356 kHz

7.3.2 Unity Gain Frequency

At input common mode voltage of 850mV

 


At input common mode voltage of 1.4V

 


Input Common Mode Voltage	Unity Gain Frequency
850mV	146.573 MHz
1.4V	148.551MHz

7.3.3 Phase Margin

At input common mode voltage of 850mV

 


At input common mode voltage of 1.4V

 


Input Common Mode Voltage	Phase Margin
850mV	61.4785deg
1.4V	61.4514deg

7.3.4 Common Mode Gain

At input common mode voltage of 850mV

 


At input common mode voltage of 1.4V

 


Input Common Mode Voltage	CM Gain
850mV	-6.353 dB
1.4V	-25.2 dB

7.3.5 PSRR

At input common mode voltage of 850mV

 

At input common mode voltage of 1.4V

 

Input Common Mode Voltage	PSRR
850mV	-4.10977 dB
1.4V	-3.82618 dB

7.4 Transient Analysis

7.4.1 Slew rate

Uncompensated Opamp

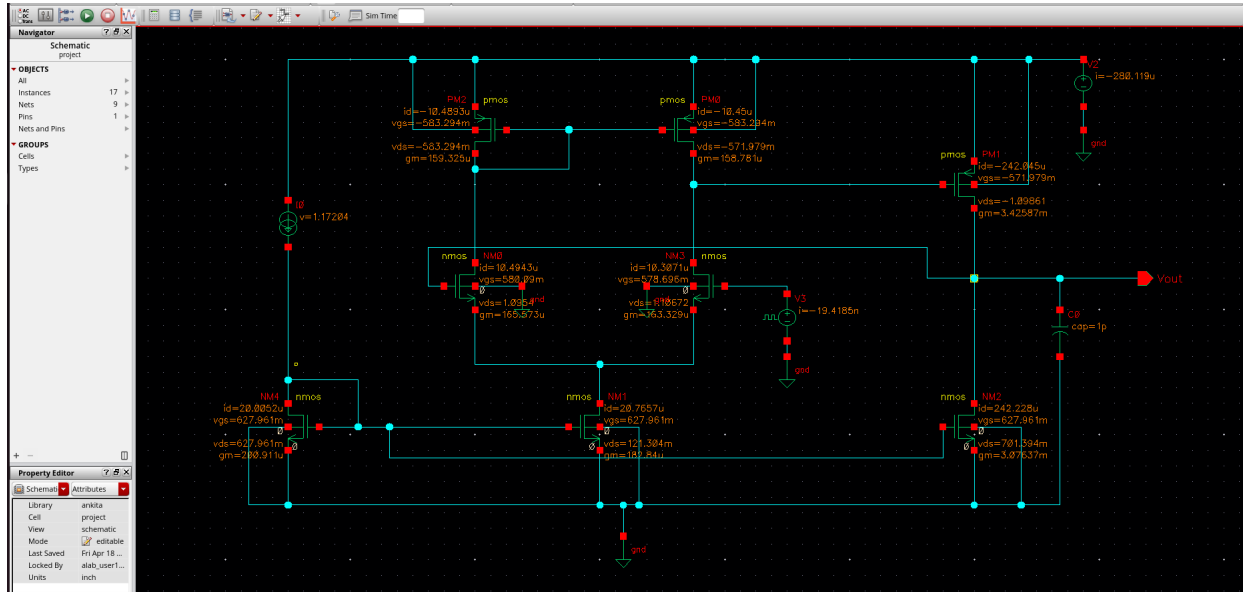


Figure 25: Schematic for transient analysis for uncompensated opamp

 


Figure 26: Transient simulation output of uncompensated op-amp

31

 


Figure 29: Slew Rate for rising edge

 


Figure 30: Slew Rate for falling edge

	Slew Rate (V/ μ s)
Rising edge	65.79
Falling edge	55.21
Total	60.5

8 Conclusion:

1. The amplifier achieved a slew rate of $60.5\text{V}/\mu\text{s}$, which is higher than the required $1\text{V}/\mu\text{s}$, indicating good dynamic performance.
2. The output swing was observed to be $156.582\text{mV} - 1.6343\text{V}$ at 850mV and $187.788\text{mV} - 1.6415\text{V}$ at 1.4V common mode voltage.
3. A phase margin of approximately 61.45° was observed, satisfying the stability criterion of $\geq 60^\circ$.
4. Input Common Mode Range (ICMR): Achieved $851\text{mV} - 1.702\text{V}$.
5. Gain: Achieved $57\text{--}59\text{dB}$, well above the minimum requirement of 40dB .
6. Gain Bandwidth Product (GBW): Achieved 161.481MHz at 850mV and 217.356MHz at 1.4V , exceeding the target of $\geq 70\text{MHz}$.
7. The unity gain frequency was recorded as 146.573MHz at 850mV and 148.551MHz at 1.4V .
8. Common Mode Gain: The common mode gain was found to be -6.353dB at 850mV and -25.2dB at 1.4V , reflecting effective common-mode signal rejection.
9. Power Supply Rejection Ratio (PSRR) values were -4.11dB at 850mV and -3.83dB at 1.4V .
10. Power Dissipation: Recorded at $581\mu\text{W}$, well below the 1mW limit.